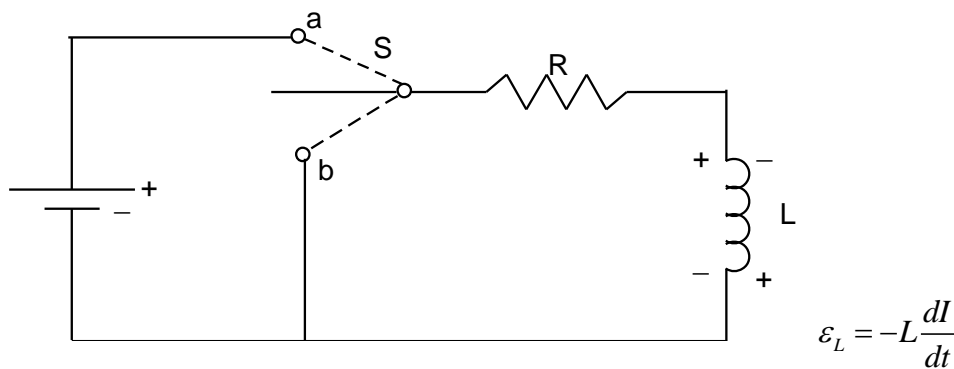


## RL Circuits

Consider the RL-Circuit shown below with the switch S initially open.



### Switch in Position 'a'

$$\sum V_{loop} = 0$$

$$V - IR - L \frac{dI}{dt} = 0$$

$$\frac{dI}{dt} = \frac{V}{L} - \frac{IR}{L}$$

At  $t=0$  when S is closed  $I = 0$ :

$$\boxed{\frac{dI}{dt} = \frac{V}{L}} \text{ At } t = 0$$

The larger the inductance  $L$ , the smaller  $dI/dt$  and the larger the opposition to the increase in current and thus the more slowly the current increases.

As  $I$  increase  $dI/dt \rightarrow 0$  and the current reaches its steady state value:

$$0 = \frac{V}{L} - \frac{IR}{L}$$

$$\boxed{I = \frac{V}{R}} \text{ Steady-state current}$$

$$\frac{dI}{dt} = \frac{VR}{LR} - \frac{IR}{L} = -\frac{R}{L} \left( I - \frac{V}{R} \right)$$


$$\int_0^I \frac{dI}{I - \frac{V}{R}} = -\frac{R}{L} \int_0^t dt$$

$$\ln \left( I - \frac{V}{R} \right) \Big|_0^I = -\frac{R}{L} t$$

$$\ln \left( I - \frac{V}{R} \right) - \ln \left( -\frac{V}{R} \right) = -\frac{t}{\tau}$$


where  $\tau = \frac{L}{R}$  (time constant)
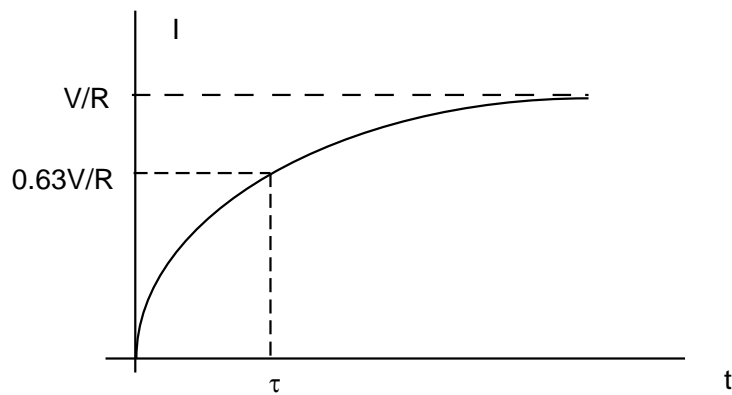
$$I(t) = \frac{V}{R} \left( 1 - e^{-\frac{t}{\tau}} \right)$$



$$\frac{dI}{dt} = -\frac{V}{R} \left( -\frac{1}{\tau} \right) e^{-\frac{t}{\tau}}$$
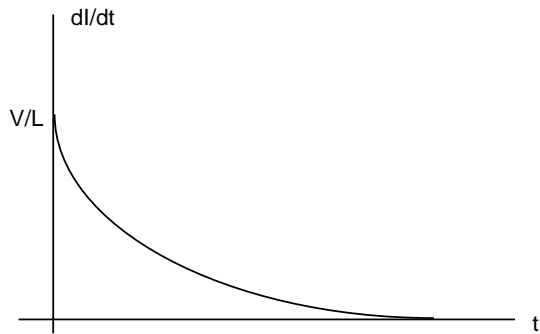
$$\boxed{\frac{dI}{dt} = \frac{V}{L} e^{-\frac{t}{\tau}}}$$




$$\varepsilon_L = -L \frac{dI}{dt}$$

$$\varepsilon_L = -L \left( \frac{V}{L} \right) e^{-\frac{t}{\tau}}$$

$$\varepsilon_L = -V e^{-\frac{t}{\tau}}$$

$$\varepsilon_L(0) = -V$$

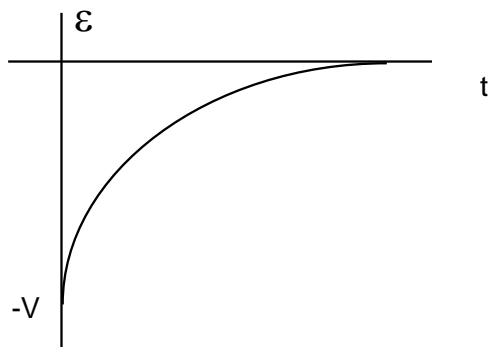

### Switch in Position 'b'

$$\sum V_{loop} = 0$$

$$-IR - L \frac{dI}{dt} = 0$$

$$\frac{dI}{I} = -\frac{R}{L} dt$$

$$\int_{V/R}^I \frac{dI}{I} = -\frac{R}{L} \int_0^t dt$$

$$I(t) = \frac{V}{R} e^{-\frac{t}{\tau}}$$

